

## A Level H2 Physics      Tutorial 14: Current of Electricity

---

Syllabus :

(a) show an understanding that electric current is the rate of flow of charge

---

(b) derive and use the equation  $I = nAvq$  for a current-carrying conductor, where  $n$  is the number density of charge carriers and  $v$  is the drift velocity

---

1.

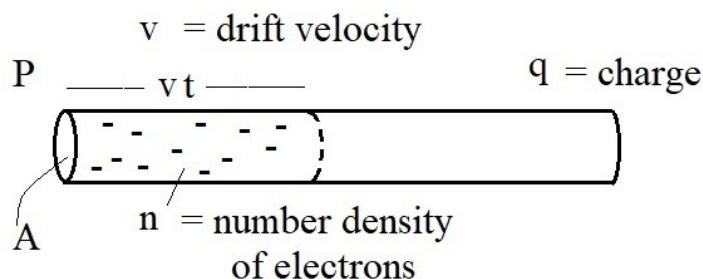


Figure 14-1

The figure shows a section of a conductor with an electric current.

The number of electrons per unit volume,  $n$ , is the electron number density. In time  $t$ , the electrons fill a length of  $vt$ , where  $v$  is the drift velocity.  $A$  is the cross-section of the wire.

- (i) In a time  $t$ , the mobile electrons fill a length  $vt$ . Write down the expression for the volume it fills.
- (ii) Write down the expression for the number of electrons that crossed the start of the wire.
- (iii) Write down the expression for the total charge of these electrons.
- (iv) Show that the current is given by  $I = nAve$ .

---

(c) recall and solve problems using the equation  $Q = It$

---

2. A cell is connected directly to a light bulb in a simple circuit. An electric current of 0.1 A flows through a light bulb. Find the amount of electric charge that flows through the bulb in 5 s.

---

(d) recall and solve problems using the equation  $V = W/Q$

---

3. For the circuit in the previous question, the cell voltage is 1.5 V. Find the work done by the cell on the bulb in 5 s.

---

(e) recall and solve problems using the equations  $P = VI$ ,  $P = I^2R$  and  $P = V^2 / R$

---

4. Find the electrical power dissipated at the bulb in the previous question.

(In English, “dissipate” means disappear. In physics, it has a similar meaning, but with the understanding that the energy is converted to other forms.)

---

(f) define the resistance of a circuit component as the ratio of the potential difference across the component to the current passing through it and solve problems using the equation  $V = IR$

---

5.

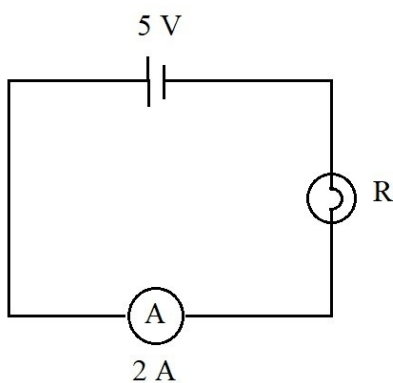


Figure 14-2

Find the resistance of the light bulb in the circuit above.

---

(g) sketch and explain the I–V characteristics of various electrical components such as an ohmic resistor, a semiconductor diode, a filament lamp and a negative temperature coefficient (NTC) thermistor

---

6. (a) For each of the following, draw the circuit symbol and explain the I-V characteristics :

- (i) ohmic resistor
- (ii) semiconductor diode
- (iii) filament lamp
- (iv) thermistor

(b) Draw the circuit symbol a light dependent resistor (LDR). Briefly describe how it works.

---

(h) sketch the resistance-temperature characteristic of an NTC thermistor

---

7. An NTC thermistor has a resistance the decreases as temperature goes up.

- (i) Sketch a graph of voltage against current to show this behaviour.
- (ii) Sketch the resistance-temperature characteristic of an NTC thermistor.

---

(i) recall and solve problems using the equation  $R = \rho l / A$

---

8. The resistance  $R$  of a wire is related to its length  $l$  and cross-sectional area  $A$  by  $R = \rho l / A$ , where  $\rho$  is a constant,  $l$  the length of the wire and  $A$  the cross-sectional area.

$\rho$  is called resistivity. Its value depends on the material of the conductor. For example, the resistivity of copper is  $1.68 \times 10^{-8} \Omega \cdot \text{m}$

Using the formula above, find the resistance of a copper wire of length 1 m and cross-sectional area  $1 \text{ cm}^2$ .

---

(j) distinguish between electromotive force (e.m.f.) and potential difference (p.d.) using energy considerations

---

9. A battery with e.m.f. 1.5 V is connected to a  $3\Omega$  filament light bulb. The current is 0.3 A.

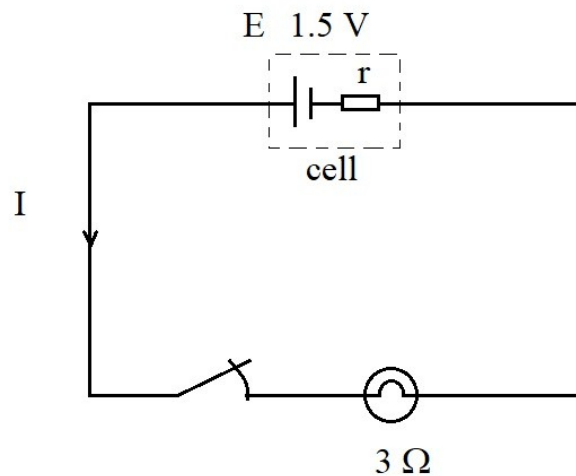


Figure 14-3

- (i) Find the potential difference across the cell.
- (ii) Why is the different from the cell emf ?
- (iii) Find the internal resistance of the cell.
- (iv) Find the power dissipated by the internal resistance.

---

(k) show an understanding of the effects of the internal resistance of a source of e.m.f. on the terminal potential difference and output power.

---

10.

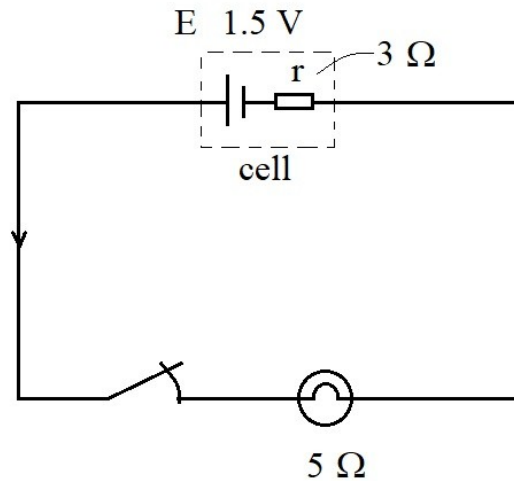


Figure 14-3

A cell has EMF  $E = 1.5 \text{ V}$  and internal resistance  $r = 3 \Omega$ . It is connected to a filament light bulb with a  $5 \Omega$  resistance.

Find :

- (i) the terminal potential difference of the cell, and
- (ii) the output power of the cell.

What would the answers be if there is no internal resistance?

*Updated 23 Feb 2025*