

A Level H2 Physics

Tutorial 15: DC Circuits

Syllabus :

(a) recall and use appropriate circuit symbols as set out in the ASE publication Signs, symbols and systematics: the ASE companion to 16-19 science (2000)

1. Draw circuit symbols for :

- | | |
|-----------------------------------|----------------------------------|
| (i) wires crossed, but not joined | (ii) wires joined at junction |
| (iii) filament lamp | (iv) fuse |
| (v) resistors | (vi) variable resistors |
| (vii) potential divider | (viii) light sensitive resistors |
| (ix) thermistor | (x) light emitting diode |
| (xi) switch (open) | (xii) voltmeters |
| (xiii) ammeters | (xiv) galvanometer |

(b) draw and interpret circuit diagrams containing sources, switches, resistors, ammeters, voltmeters, and/or any other type of component referred to in the syllabus

2. Draw a circuit diagram containing :

- a cell of 1.5 V, with internal resistance $3\ \Omega$
- a lamp with resistance $8\ \Omega$
- a voltmeter across the lamp only
- an ammeter

(c) solve problems using the formula for the combined resistance of two or more resistors in series

3.

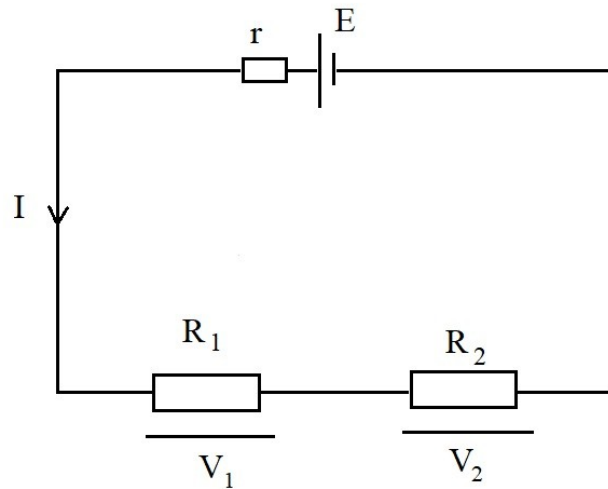


Figure 15-1

Using Ohm's law and the definition of voltage, show that the combined resistance of R_1 and R_2 is $R_1 + R_2$.

(d) solve problems using the formula for the combined resistance of two or more resistors in parallel

4.

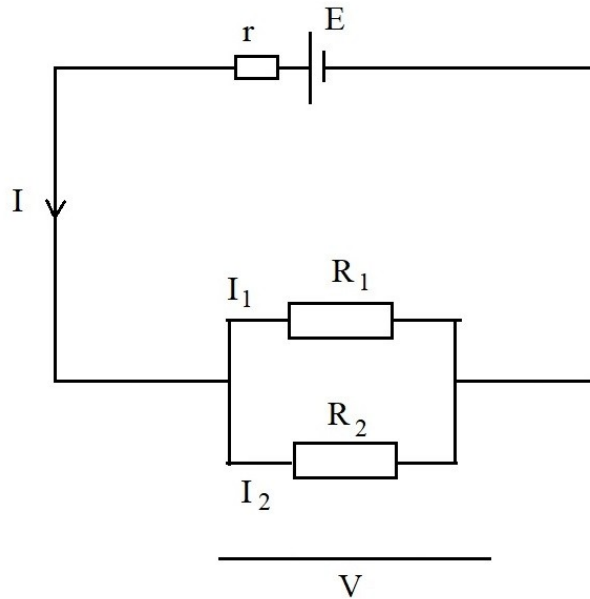


Figure 15-2

Using Ohm's law and the definition of current, show that the combined resistance of R_1 and R_2 is R , where

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

(e) solve problems involving series and parallel circuits for one source of e.m.f.

5.

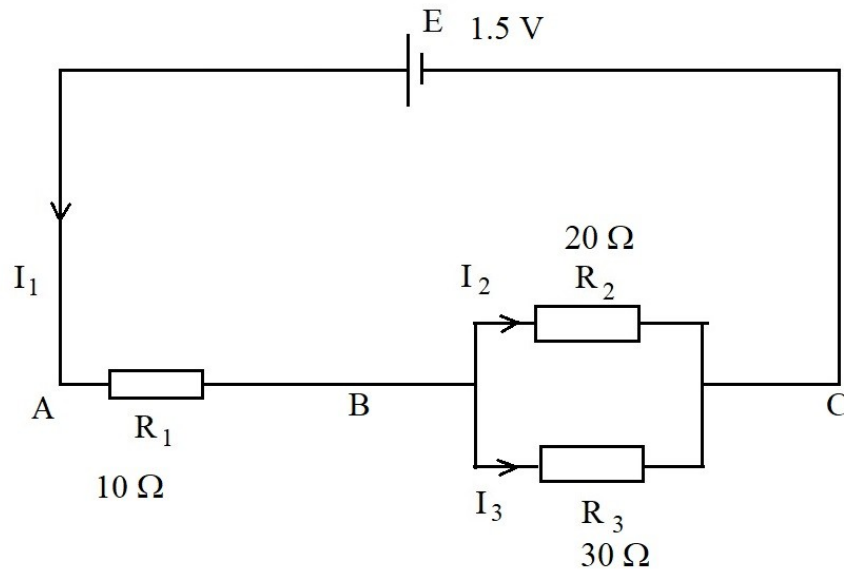


Figure 15-3

- (i) Find the combined resistance between B and C.
- (ii) Find the combined resistance between A and C.
- (iii) Find the currents I₁, I₂, and I₃.

(f) show an understanding of the use of a potential divider circuit as a source of variable p.d.

6.

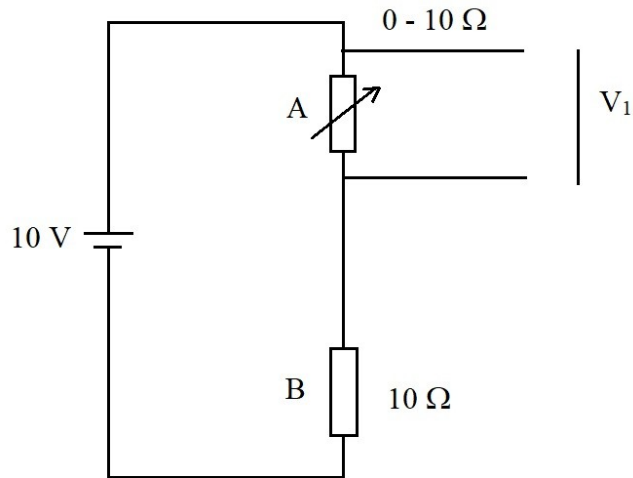


Figure 15-4

(a) What is the voltage V_1 when A is

- (i) $0\ \Omega$
- (ii) $10\ \Omega$

(b) If a light bulb is connected across A, what would be the effect as A is adjusted from 0 to $10\ \Omega$.

(g) explain the use of thermistors and light-dependent resistors in potential divider circuits to provide a potential difference which is dependent on temperature and illumination respectively

7. The resistance of a thermistor decreases when it gets hot, like if there is a fire.

Assume that the resistance-temperature R - θ graph is a straight line.

$\theta / \text{deg C}$	$R / \text{k}\Omega$
21	5.9
100	0.31

This figure shows a simple fire alarm circuit.

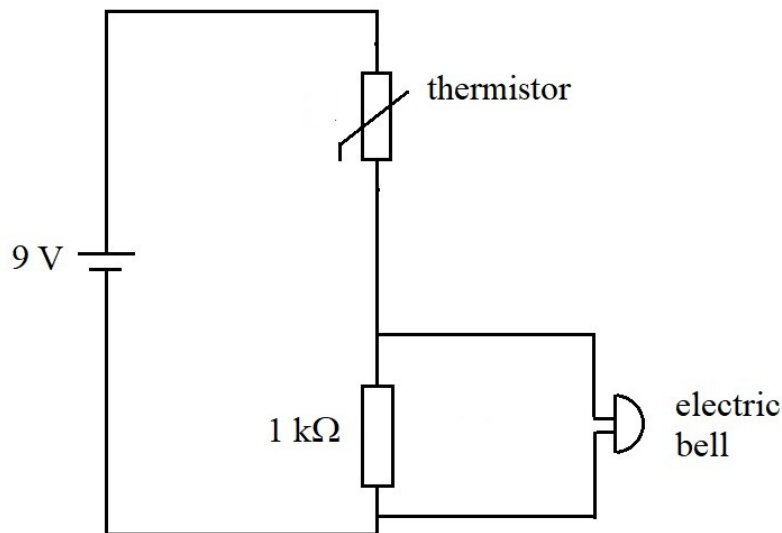


Figure 15-5

The electric bell rings when its voltage is over 5 V.

Estimate the temperature when it rings.

(h) recall and solve problems by using the principle of the potentiometer as a means of comparing potential differences.

8 (a)

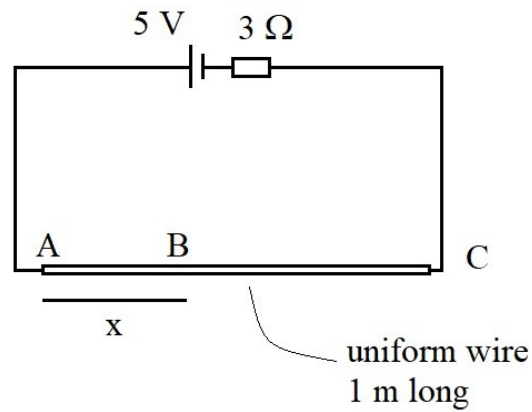


Figure 15-6

- (i) What is the voltage across AC?
- (ii) If x is 30 cm, what is the voltage across AB?

(b)

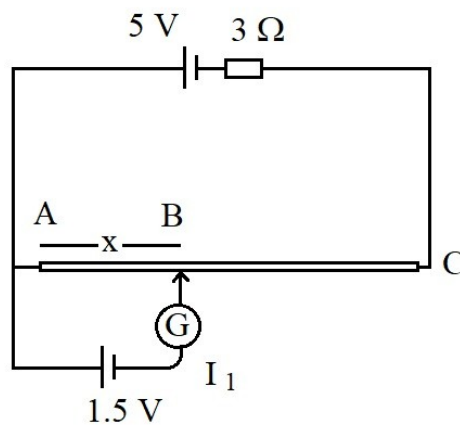


Figure 15-6

- (i) A cell of emf 1.5 V is connected as shown. What is the current I_1 ?
 - (ii) Does I_1 increase or decrease if this cell has an internal resistance? Why?
- (c)
- (i) Suggest how this setup (called a potentiometer) can be used to measure emf?
 - (ii) What advantage does it have over a voltmeter?

Updated 23 February 2025